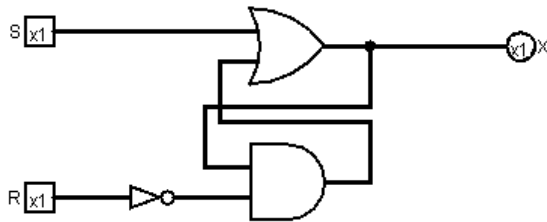


# Computer Science

## Set-Reset Flip-Flop Representations

Circuit



Truth Table


Row for every input combination for each initial state  
 Optionally show state transitions with arrows

State (X)	S	R	New State (X)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



State Diagram

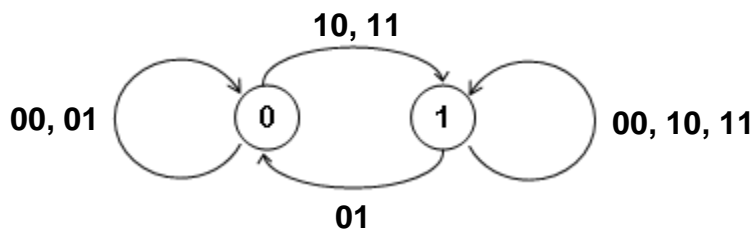States represented as circles (nodes)  
 Every input combination for each state shows resulting state



Summary

Describes what happens to state for each input combination

S	R	X
0	0	Unchanged
0	1	Sets to 0
1	0	Sets to 1
1	1	Sets to 1