

# *Digital Logic*

How to do something useful with all  
those 1s and 0s




# *Processing 1s and 0s*


- Logic “Gates” (electronics)
- Truth Tables (logic)
- Boolean Expressions (algebra)



# *NOT Gate aka "Inverter"*

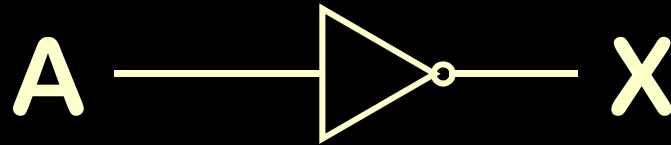

# *NOT Gate aka "Inverter"*

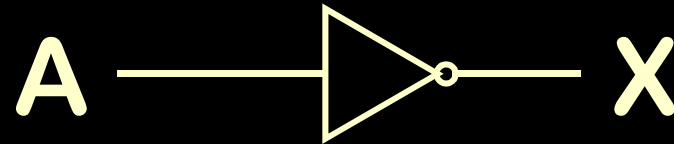


A	X
0	1
1	0

Truth Table



# *NOT Gate aka "Inverter"*

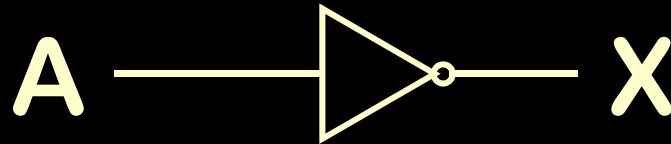

$$X = \bar{A}$$


A	X
0	1
1	0

Boolean Algebra

Truth Table



# *NOT Gate aka "Inverter"*

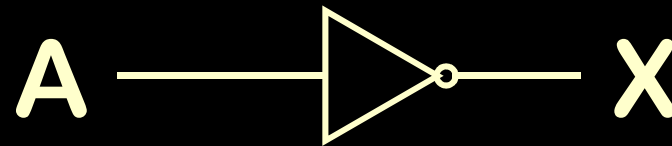

$$X = \bar{A}$$

$$X = A'$$


A	X
0	1
1	0

Boolean Algebra

Truth Table



# *NOT Gate aka "Inverter"*

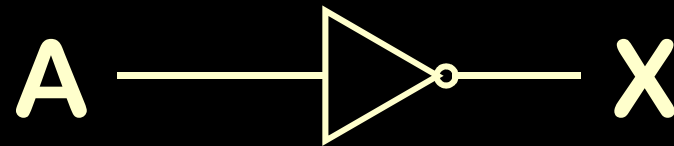

$$X = \bar{A}$$

$$X = A'$$

$$X = !A$$


A	X
0	1
1	0

Boolean Algebra

Truth Table



# AND Gate

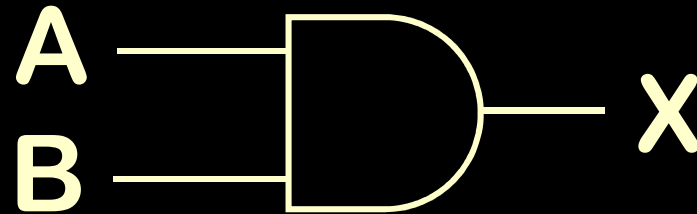

$$X = A \cdot B$$


$$X = AB$$

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1





# OR Gate

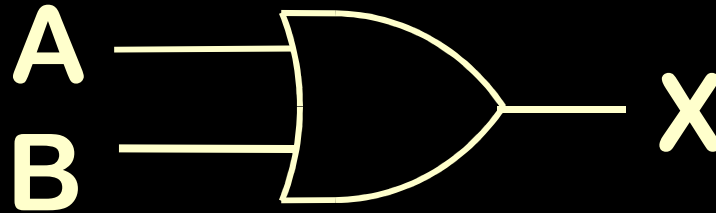


$$X = A + B$$

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1



# *Combinational Circuits*

$$A(B + C)$$

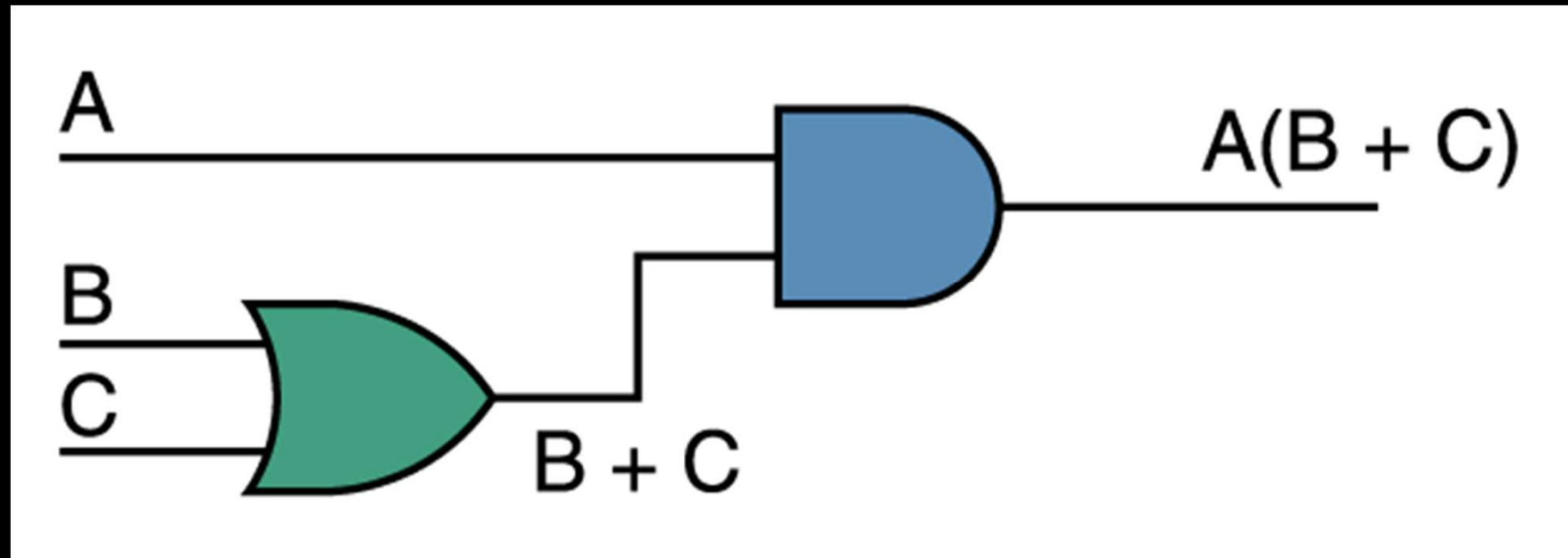

# *Combinational Circuits*

$$A(B + C)$$

<b>A</b>	<b>B</b>	<b>C</b>	<b>B+C</b>	<b>A(B+C)</b>
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



# *Combinational Circuits*

$$A(B + C)$$

A	B	C	B+C	A(B+C)
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		



# *Combinational Circuits*

$$A(B + C)$$

A	B	C	B+C	A(B+C)
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	1	
1	1	0	1	
1	1	1	1	



# *Combinational Circuits*

$$A(B + C)$$

A	B	C	B+C	A(B+C)
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	1	
1	1	0	1	
1	1	1	1	



# *Combinational Circuits*

$$A(B + C)$$

A	B	C	B+C	A(B+C)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1



# Combinational Circuits


$$A(B + C)$$

A	B	C	B+C	A(B+C)
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	0
1	0	1	1	1
1	1	0	1	1
1	1	1	1	1





# XOR Gate

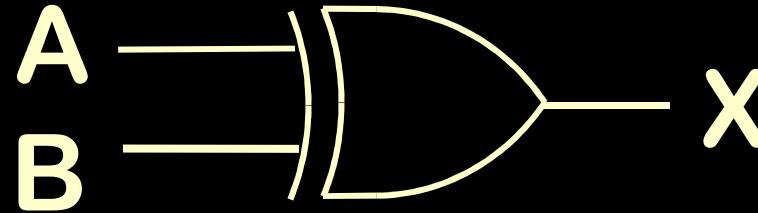

$$X = A \oplus B$$

*MS Office: Insert Symbol*

*Google: Insert → Special Characters*

$$X = A \wedge B$$

*On a standard keyboard*

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0



# NAND Gate



$$X = \overline{AB}$$


$$X = (AB)'$$

$$X = !(AB)$$

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0



# NOR Gate

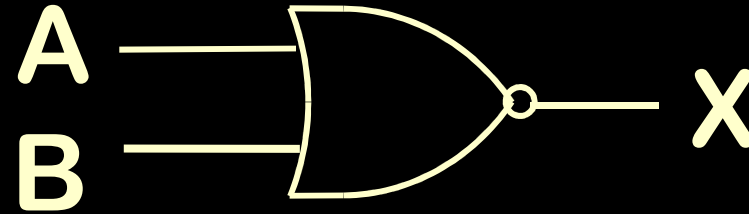

$$X = \overline{A+B}$$

$$X = (A+B)'$$


$$X = !(A+B)$$

A	B	X
0	0	1
0	1	0
1	0	0
1	1	0



# *Combinational Circuits*

$(AB + AC)$

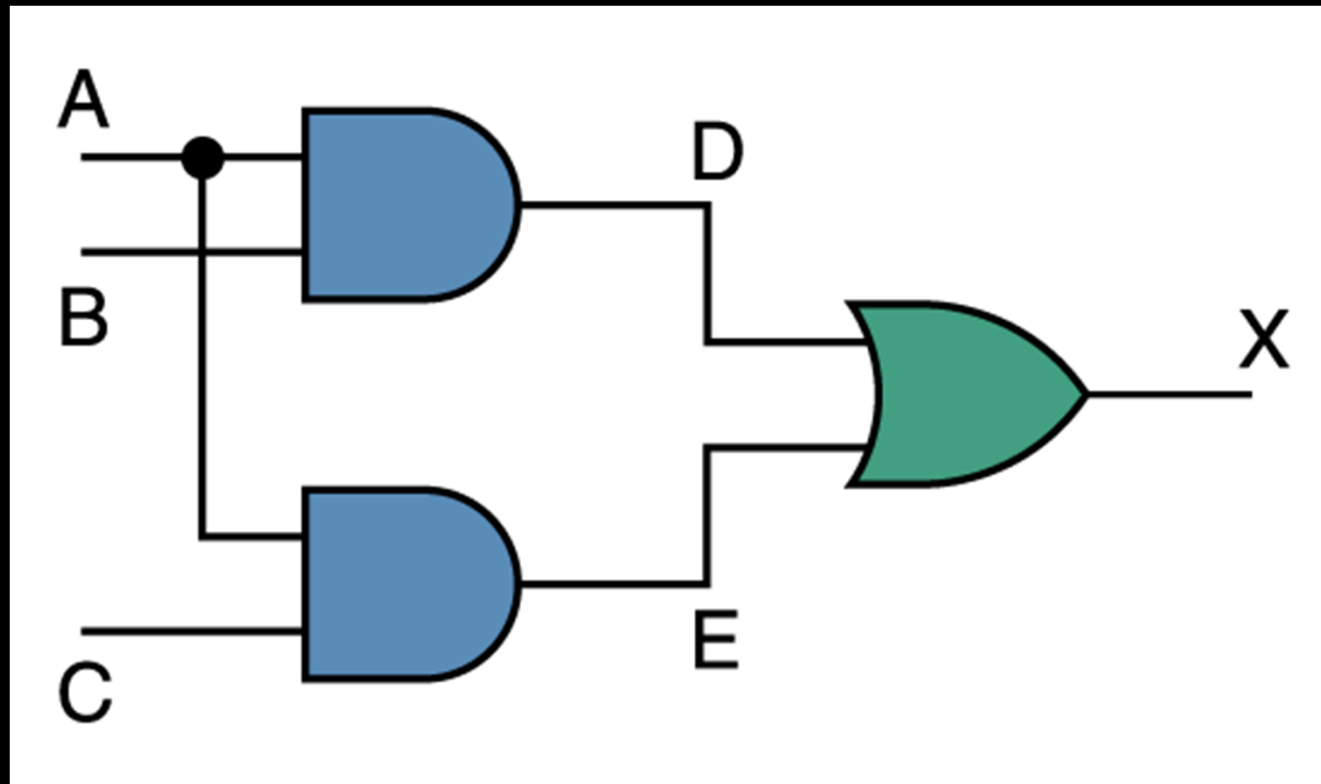

# *Combinational Circuits*

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			



# *Combinational Circuits*

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			



# *Combinational Circuits*

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0	0		
0	0	1	0		
0	1	0	0		
0	1	1	0		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		



# *Combinational Circuits*

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0	0		
0	0	1	0		
0	1	0	0		
0	1	1	0		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		





# *Combinational Circuits*

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0	0	0	
0	0	1	0	0	
0	1	0	0	0	
0	1	1	0	0	
1	0	0	0	0	
1	0	1	0	1	
1	1	0	1	0	
1	1	1	1	1	



# *Combinational Circuits*

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0	0	0	
0	0	1	0	0	
0	1	0	0	0	
0	1	1	0	0	
1	0	0	0	0	
1	0	1	0	1	
1	1	0	1	0	
1	1	1	1	1	



# *Combinational Circuits*

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1



# Combinational Circuits

$$(AB + AC)$$

A	B	C	AB	AC	AB+AC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1



# Combinational Circuits


$$(AB + AC) = A(B + C)$$

A	B	C	AB	AC	AB+AC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	0	1	1
1	1	1	1	1	1



# *Equivalent Circuits*

$$(AB + AC) = A(B + C)$$

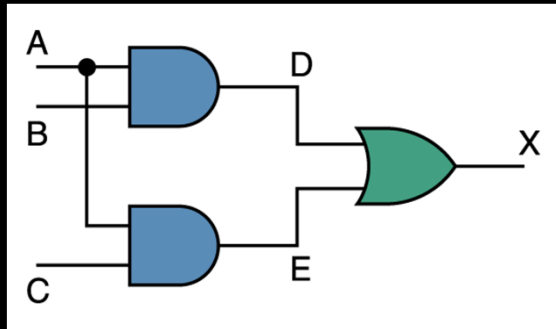

=

